

Name: **Samrathpreet Singh Randhawa**

Roll No.: **1801CS43**

CS-226 (Switching Theory Lab)

Lab-8

Question 0) Basic sequential elements J-K, Q and D flip flops.

JK Flip Flop


Clock	J	K	Q(t)	Q'(t)	State
0	X	X	Q(t-1)	Q'(t-1)	Memory
1	0	0	Q(t-1)	Q'(t-1)	Memory
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	Q'(t-1)	Q(t-1)	Toggle


Truth Table

JK Flip Flop

Test Case:

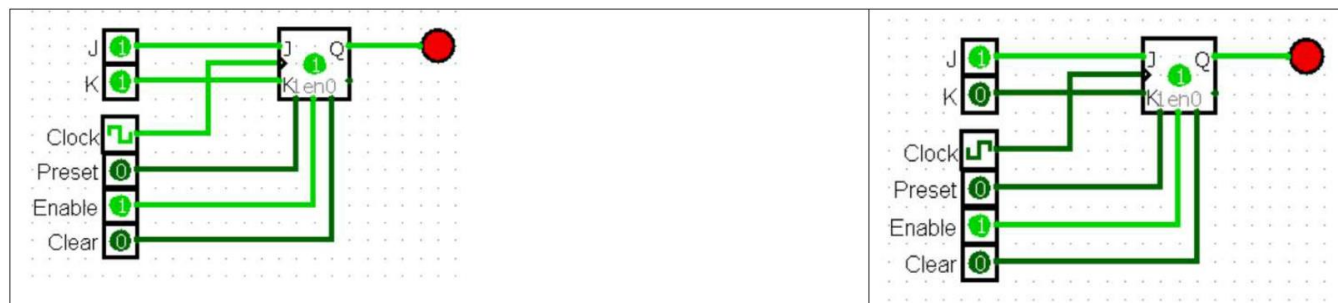1. Set J = 1, K = 1 followed by Clock = 1, notice Value stored = 1 (Set State)
2. Set Clock = 0, change J and K randomly, no change in Value stored (Memory State)
3. Set J = 0, K = 1, then Clock = 1, notice Value stored = 0 (Reset State)
4. Set Clock = 0
5. Set J = 1, K = 1, and keep toggling the clock, notice value stored also toggles (Toggle State)




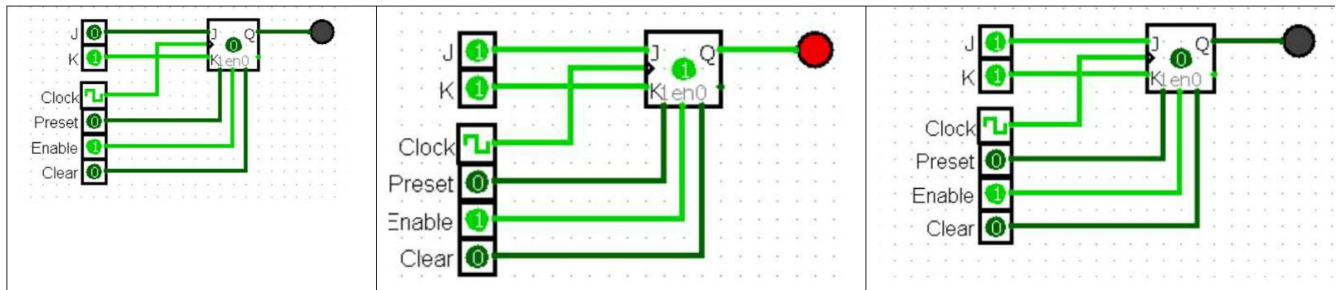

SR Flip Flop


Clock	S	R	Q(t)	Q'(t)	State
0	X	X	Q(t-1)	Q'(t-1)	Memory
1	0	0	Forbidden		
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	Q(t-1)	Q'(t-1)	Memory


Truth Table

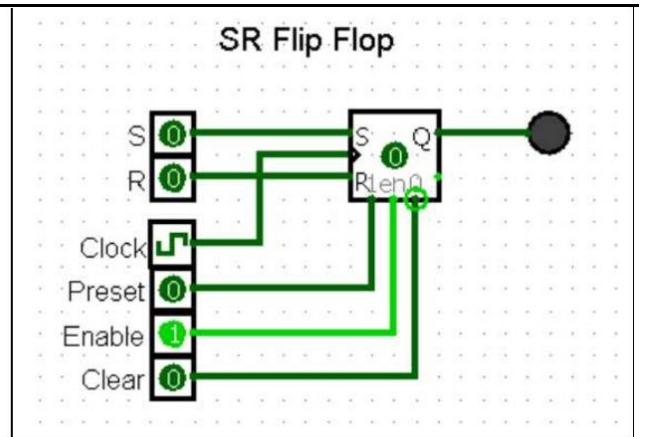

Test Case:

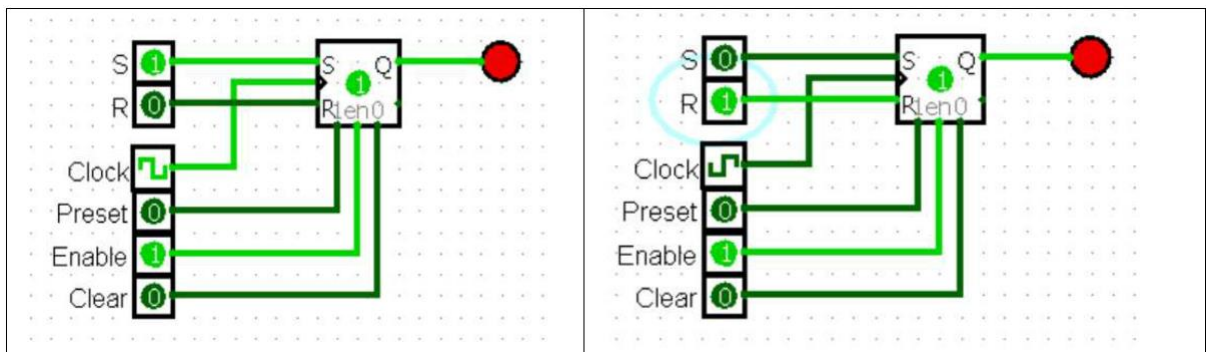1. Set S = 1, followed by Clock = 1, notice Value stored = 1 (Set State)
2. Set Clock = 0, change S and R randomly, no change in Value stored (Memory State)
3. Set S = 0, R = 1, then Clock = 1, notice Value stored = 0 (Reset State)
4. Set Clock = 0
5. Set S = 1, R = 1, then Clock = 1, no change in Value stored (Memory State)




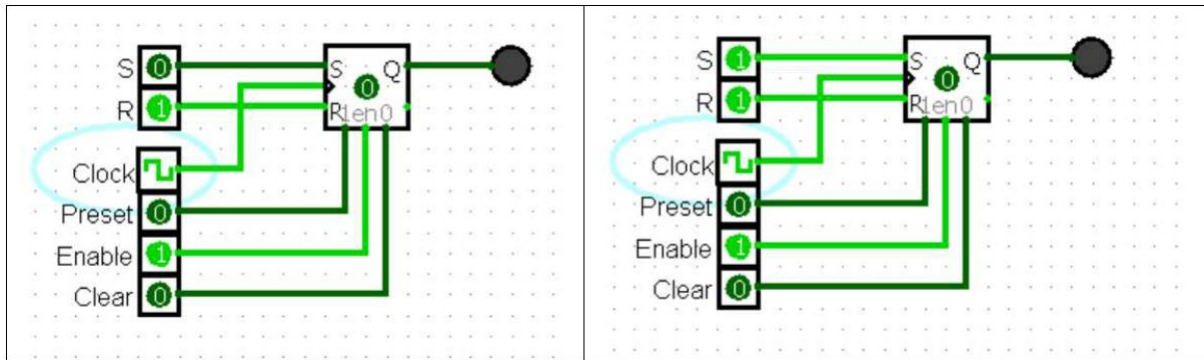

D Flip Flop


Clock	D	Q(t)	State
0	X	Q(t-1)	Memory
1	0	0	Reset
1	1	1	Set

Truth Table

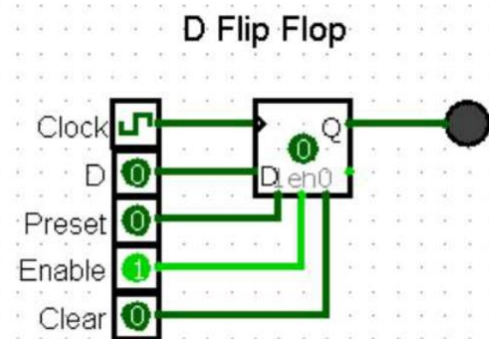

Test Case:

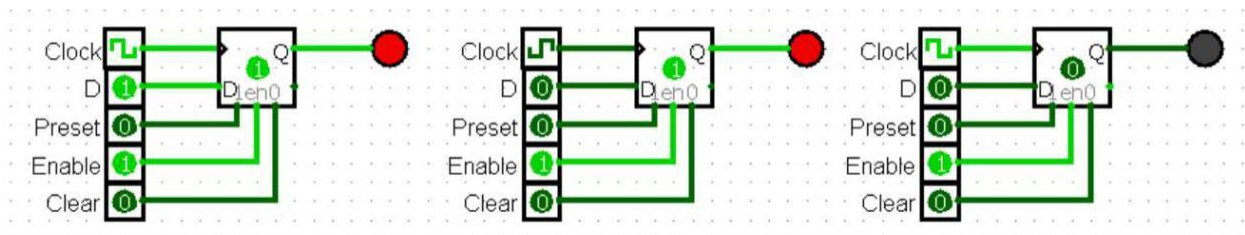
1. Set Clock = 1, D = 1, notice Value Stored = 1
2. Set Clock = 0, Value stored doesn't change on changing D (Memory)
3. Set D = 1, Clock = 1, notice Value Stored = 1



T Flip Flop


Clock	T	Q(t)	State
0	X	Q(t-1)	Memory
1	0	Q(t-1)	Memory
1	1	Q'(t-1)	Toggle

Truth Table

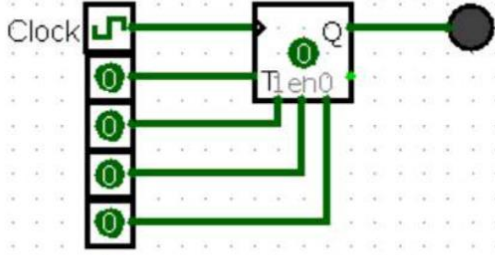


Test Case:


1. Set Clock = 1, T = 0, notice no change in Value Stored
2. Set Clock = 0, Value stored doesn't change on changing T (Memory)
3. Set T = 1, Clock = 1, and keep toggling the clock, notice Value stored also toggles

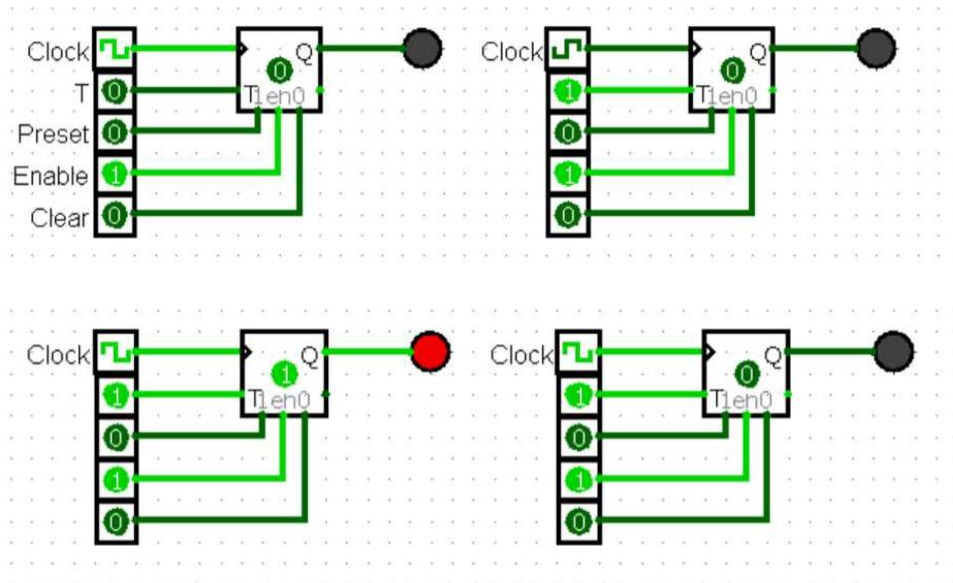

Question 1) 8 Bit Shift Register using flipflop is implemented in file p1. circ

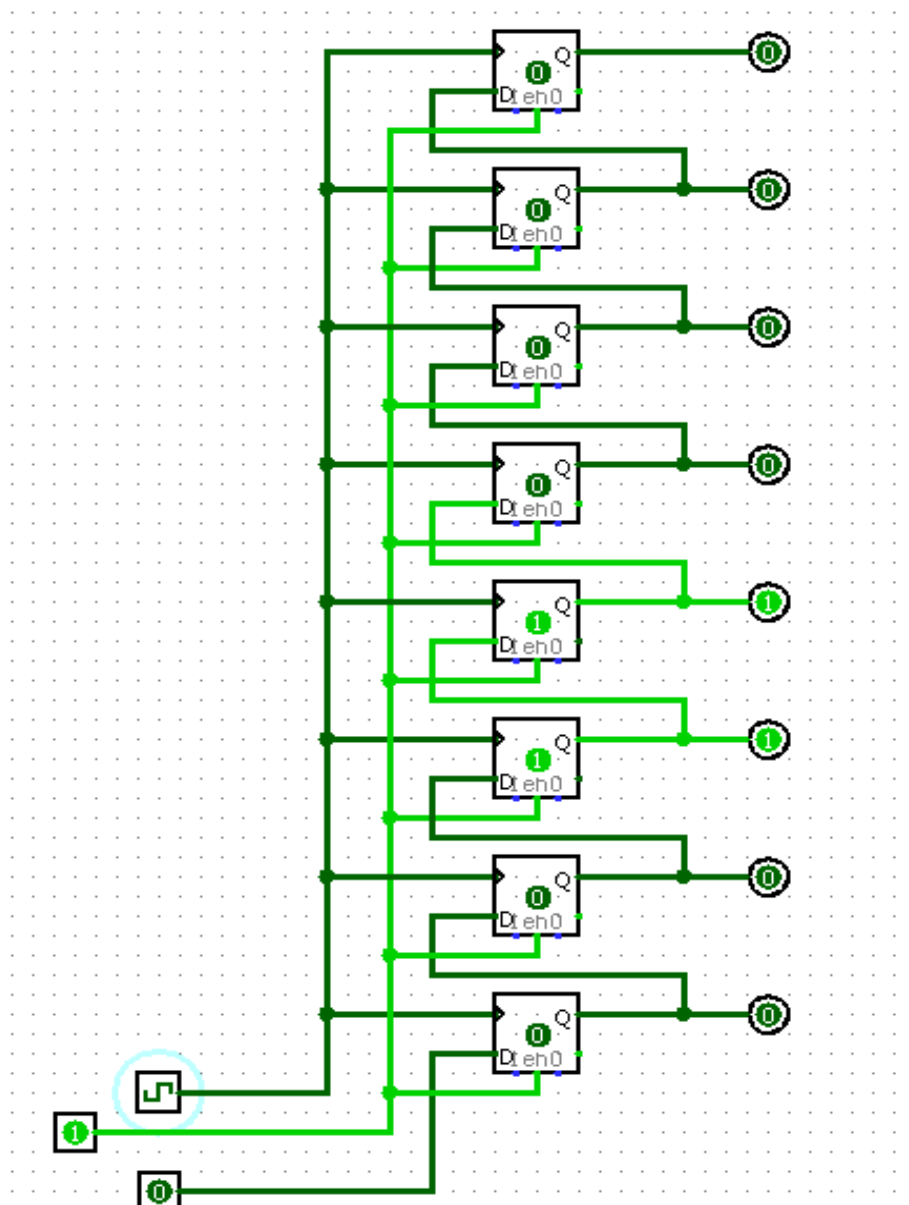


Question 2) Simulated 4-bit Parallel Input Parallel Output (PIPO) register and submitted in p2. circ

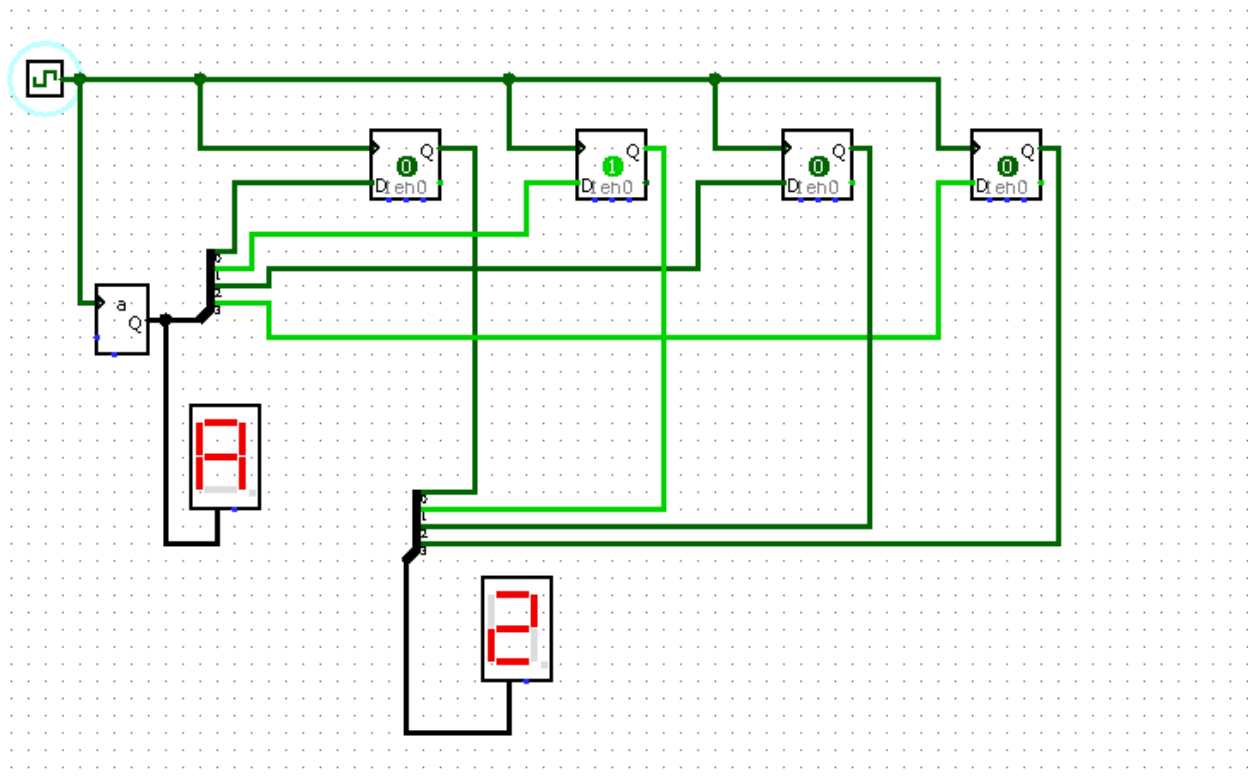


Question 3) Submitted in p3. circ

4 Bit counter using T-Flip Flops

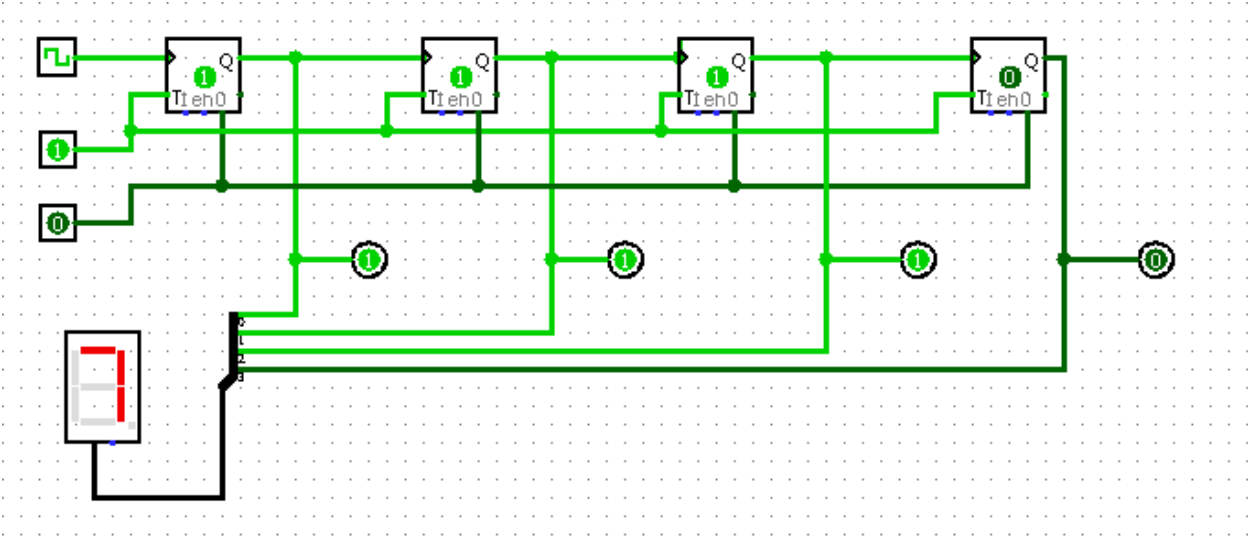


6 Bit counter using T-Flip Flops

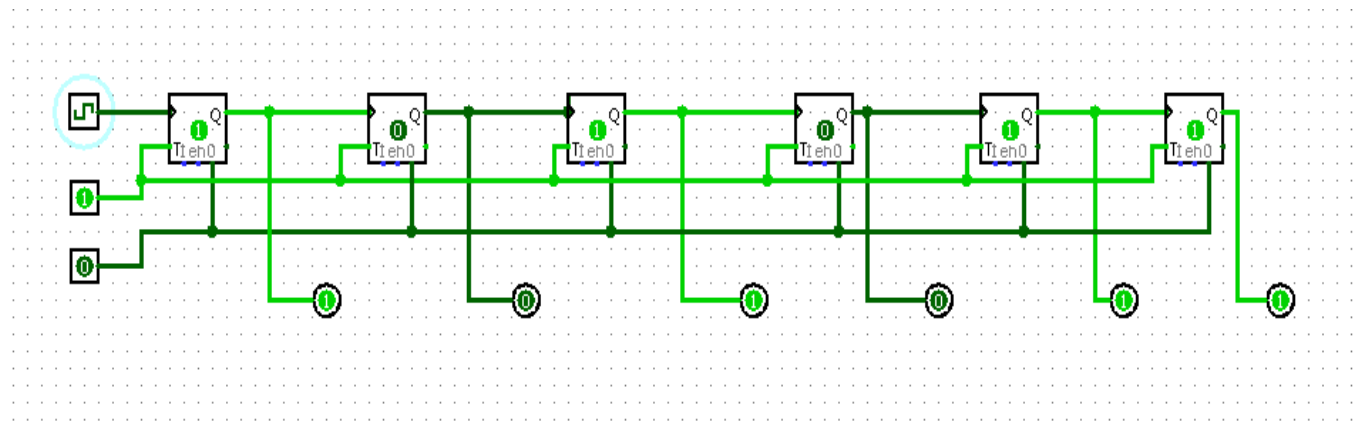


Question 4) Simulated 8-bit Multifunction Shift register using Logisim submitted in p4. circ

4bit multi-function register

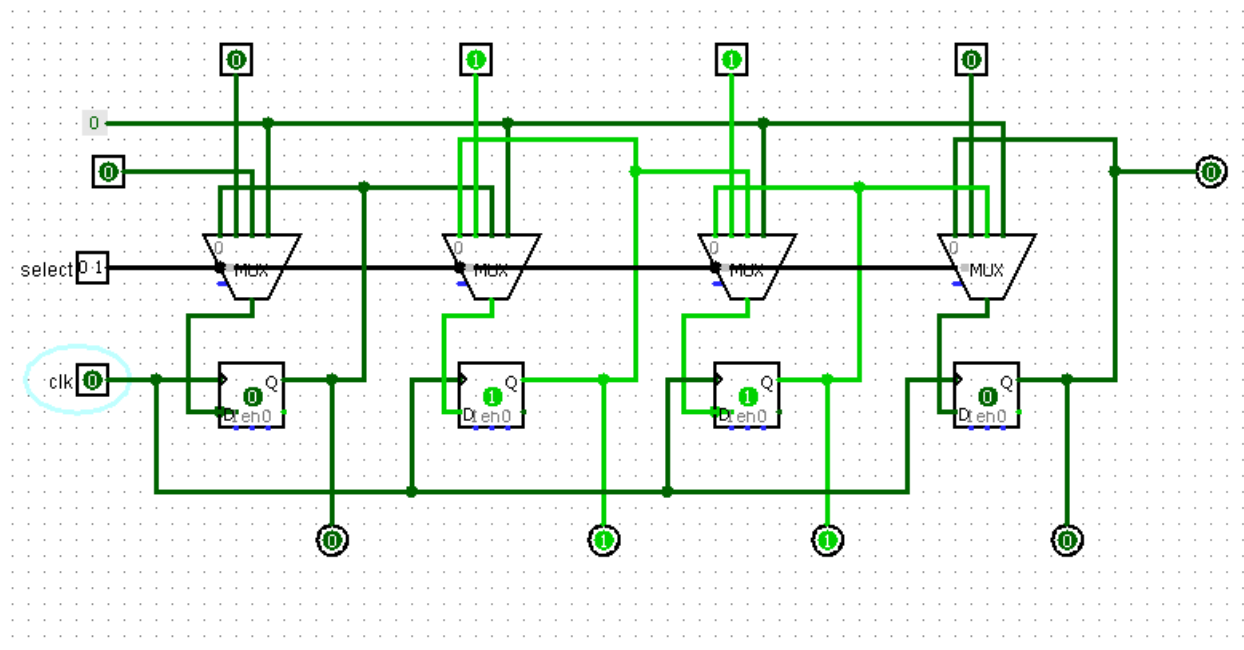

8bit version multi-function register

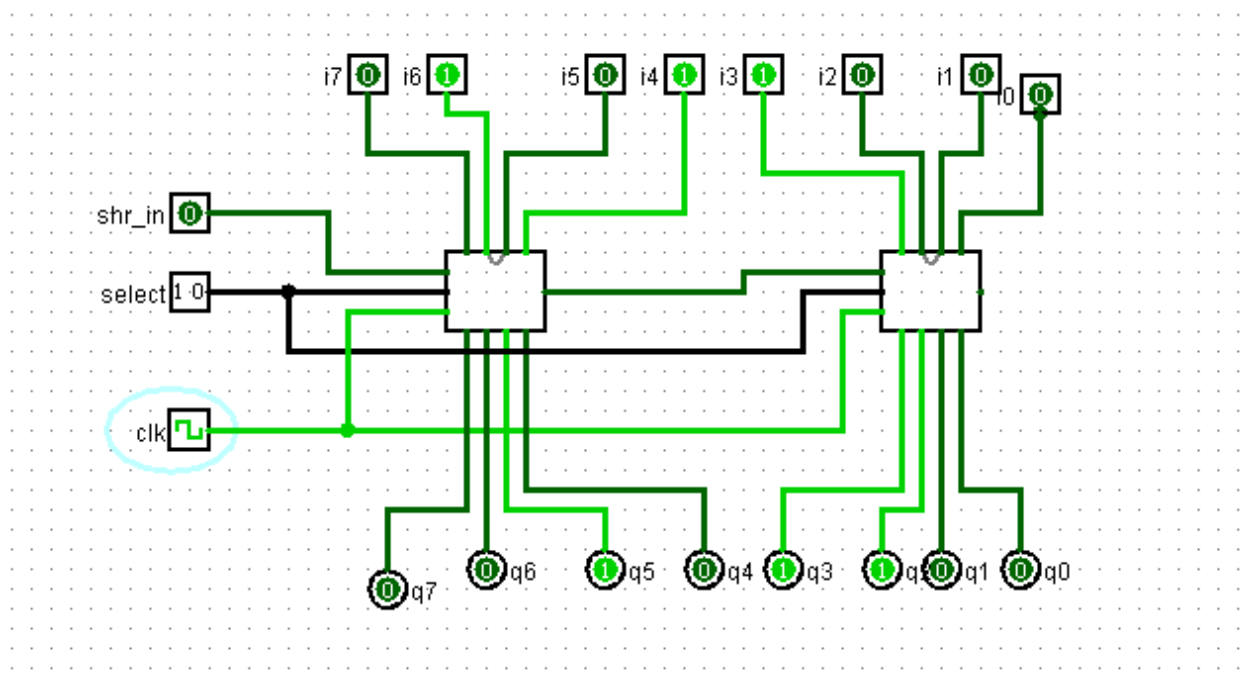

Question 5) Implemented a 16 x 16 register file submitted in p5. circ

